

Ganpat University
Faculty of Engineering & Technology
Computer Science & Engineering
2CSE205: Computer Organization

Name:- Dwij Vatsal Desai

Sem:- 2

Sub: - CO

Enrollment No.:- 23162121027

Prac:- 5

Date:- 10/4/2024

PRACTICAL - 5

AIM: To study and design Wallace Tree Adder.

THEORY:

There are many cases where it is desired to add more than two numbers together. The straightforward way of adding together m numbers (all n bits wide) is to add the first two, then add that sum to the next using cascading full adders.

The Wallace tree has three steps:

1. Multiply (that is – AND) each bit of one of the arguments, by each bit of the other, yielding n^2 results. Depending on position of the multiplied bits, the wires carry different weights, for example wire of bit carrying result of a_2b_3 is 32.
2. Reduce the number of partial products to two by layers of full and half adders.
3. Group the wires in two numbers, and add them with a conventional adder.

The second phase works as follows. As long as there are three or more wires with the same weight add a following layer:


- Take any three wires with the same weights and input them into a full adder. The result will be an output wire of the same weight and an output wire with a higher weight for each three input wires.

- If there are two wires of the same weight left, input them into a half adder.
- If there is just one wire left, connect it to the next layer.

This requires a total of $m - 1$ additions, for a total gate delay of $O(m \lg n)$ (assuming look ahead carry adders). Instead, a tree of adders can be formed, taking only $O(\lg m \cdot \lg n)$ gate delays.

A Wallace tree adder adds together n bits to produce a sum of $\log_2 n$ bits.

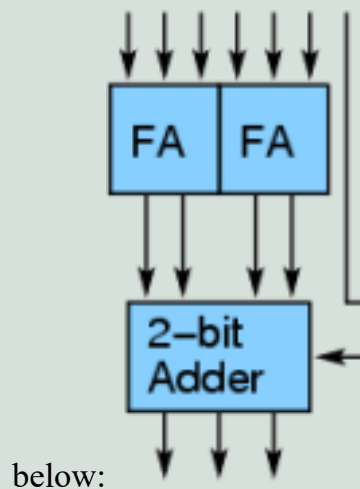Case 1: Wallace tree adder to add seven bits (W_7) is illustrated




below:

2CSE205: Computer Organization

Case 2: Wallace tree adder to add three 4-bit numbers is illustrated below:

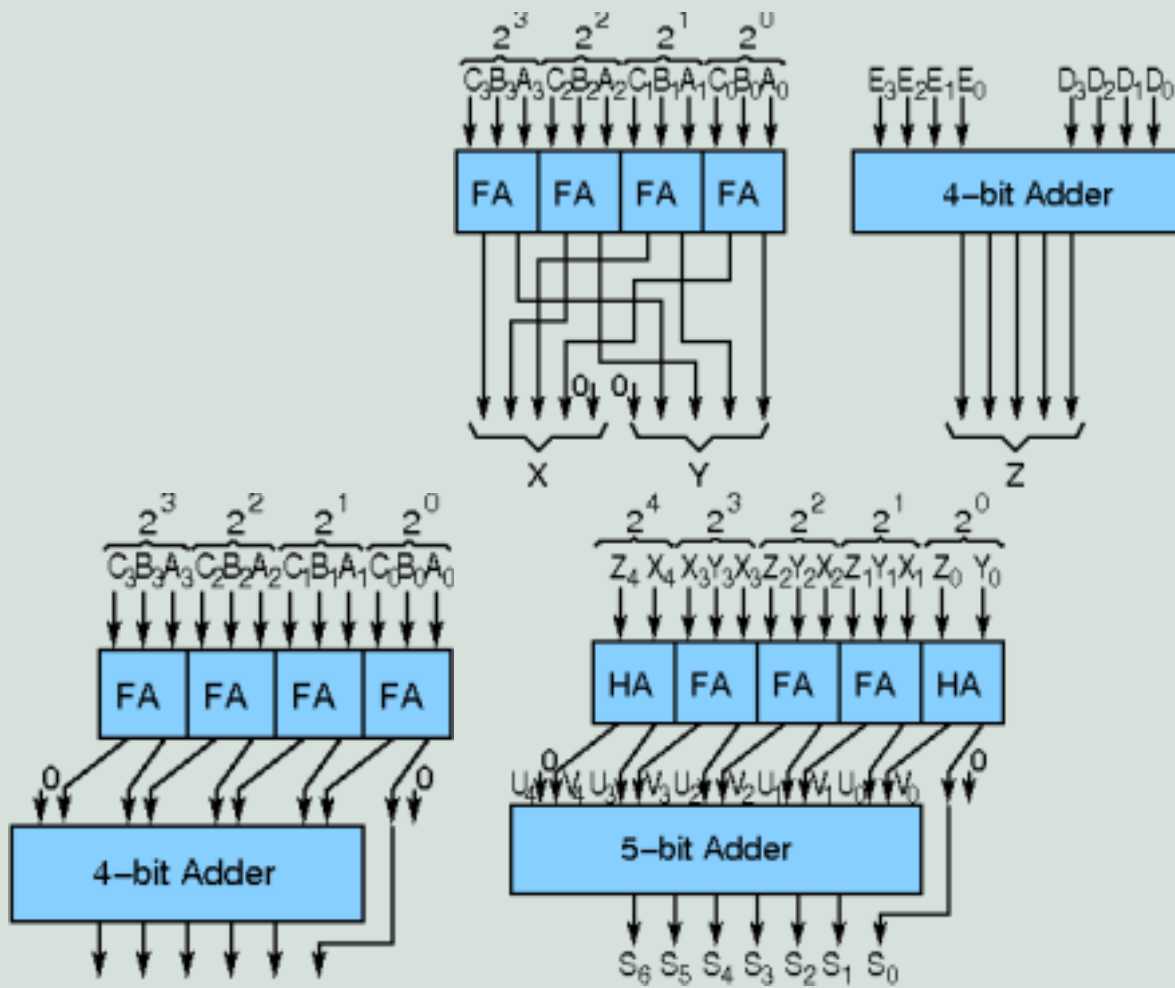Case 3: Wallace tree adder to add five 4-bit numbers is illustrated below:




Components:

1. Half Adder
2. Full Adder
3. 4-bit adder

Result: show steps for each case.


LABWORK: add extra pages

1. Addition of seven bits

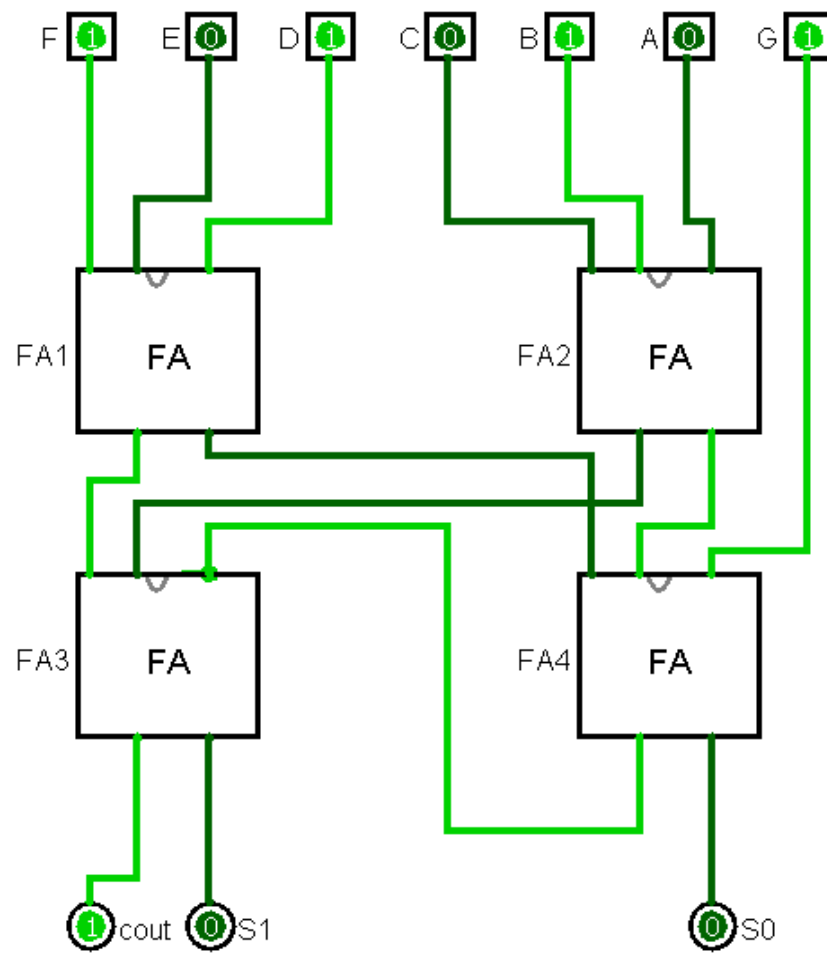


Dwij deasi 27 2nd-sem (BDA)

2. Addition of three 4-bit numbers

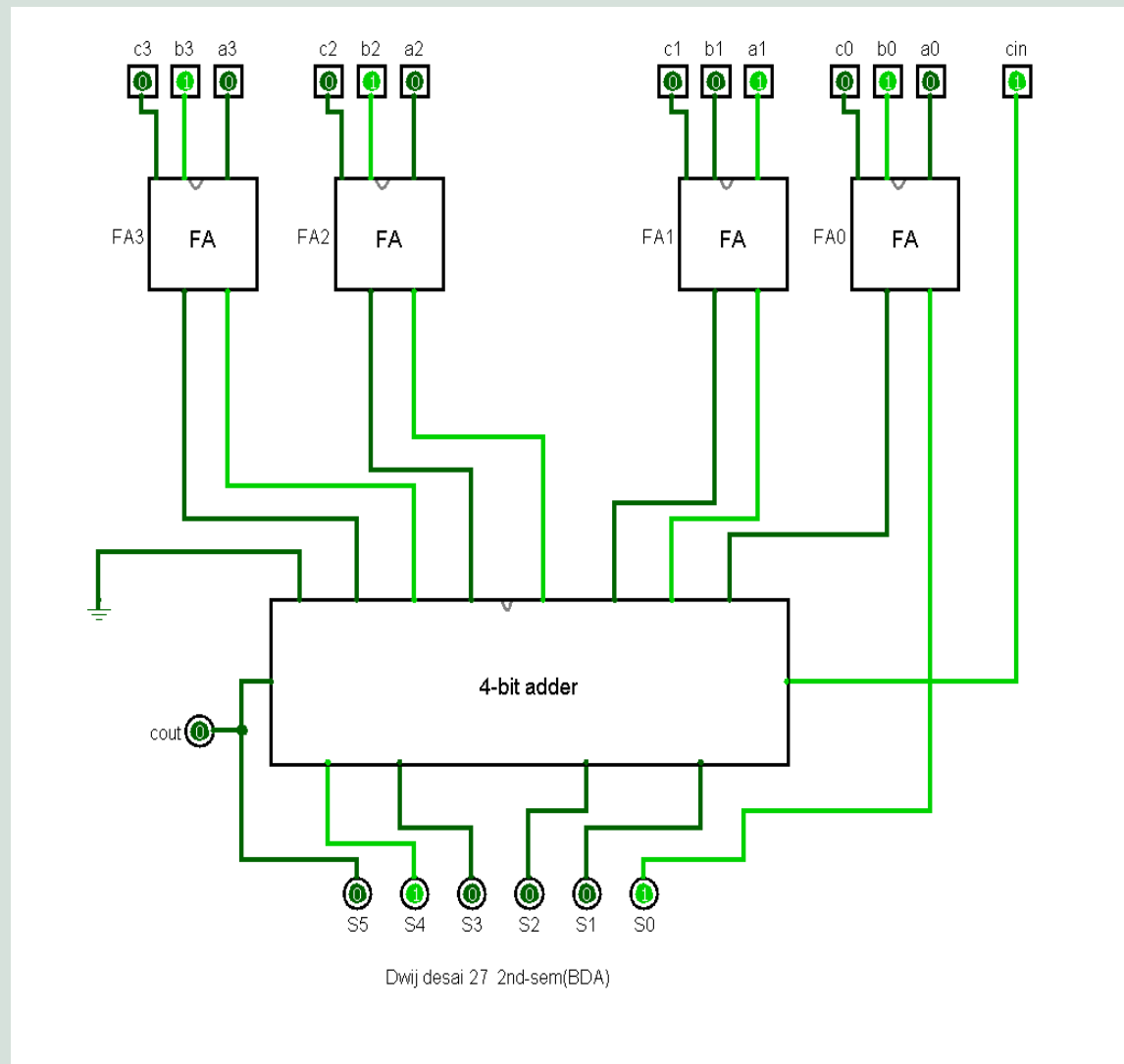

3. Addition of five 4-bit numbers

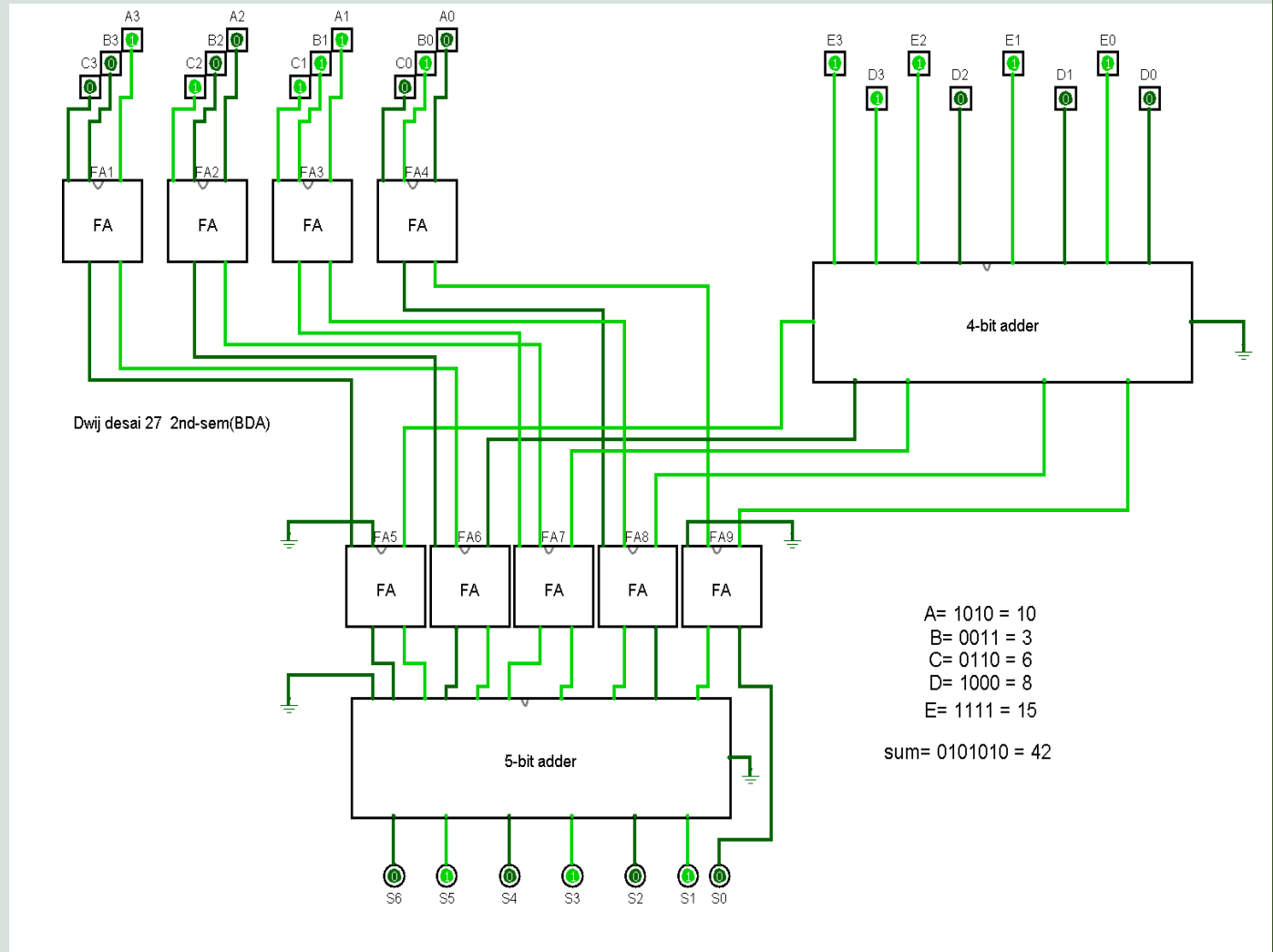

CONCLUSION:

In conclusion, Wallace tree adders are a strong contender for digital circuits where speed is paramount. Their parallel processing and efficient reduction techniques make them ideal for high-performance applications like signal processing and modern CPUs. However, for simpler tasks or situations where space and power are limited, simpler adder designs might be more suitable. Consider a scenario where a small, battery-powered device needs basic arithmetic capabilities. In this case, a Wallace tree adder's complexity and footprint might be overkill. A simpler adder, while slower, could provide adequate performance while conserving valuable space and power resources.